

Unit: 5


A/D and D/A Converter.

* Analog quantity are Continuous range of Value.

* Temperature, pressure, light etc are analog quantity.

* Digital Quantity is a Discrete quantity.

Digital to Analog Converter.

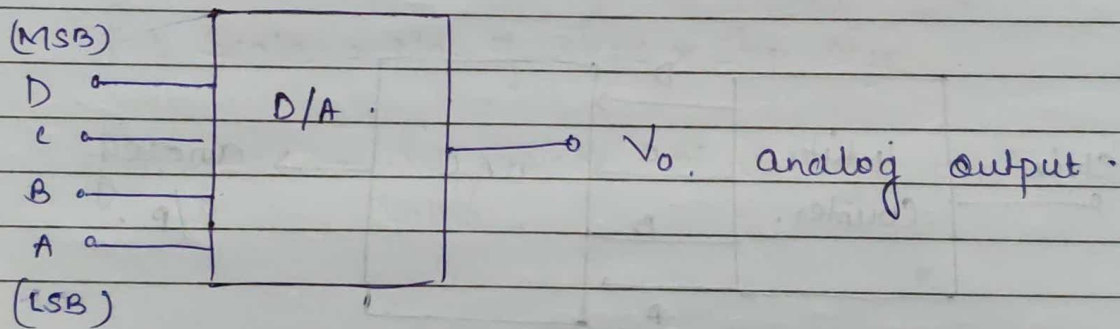

→ It convert digital number into analog.

→ The Binary number or BCD number is converted to Voltage and current.

→ 4 Input is given Thus, $2^4 = 16$ Combinational Input.

Analog Output = $k \times$ digital Input.

k = proportional factor (constant Value).



→ It do not provide a exact analog value.

→ The output of DAC = pseudo Analog Quantity.

→ No. of I/p Increase = Output Values will Increased.

= A Counter is recycle again after 16 state, then DAC o/p = staircase waveform, of 1 V.

	I/p.		O/p.
Counter :-	0000	→	0V.
	1111	→	15V.

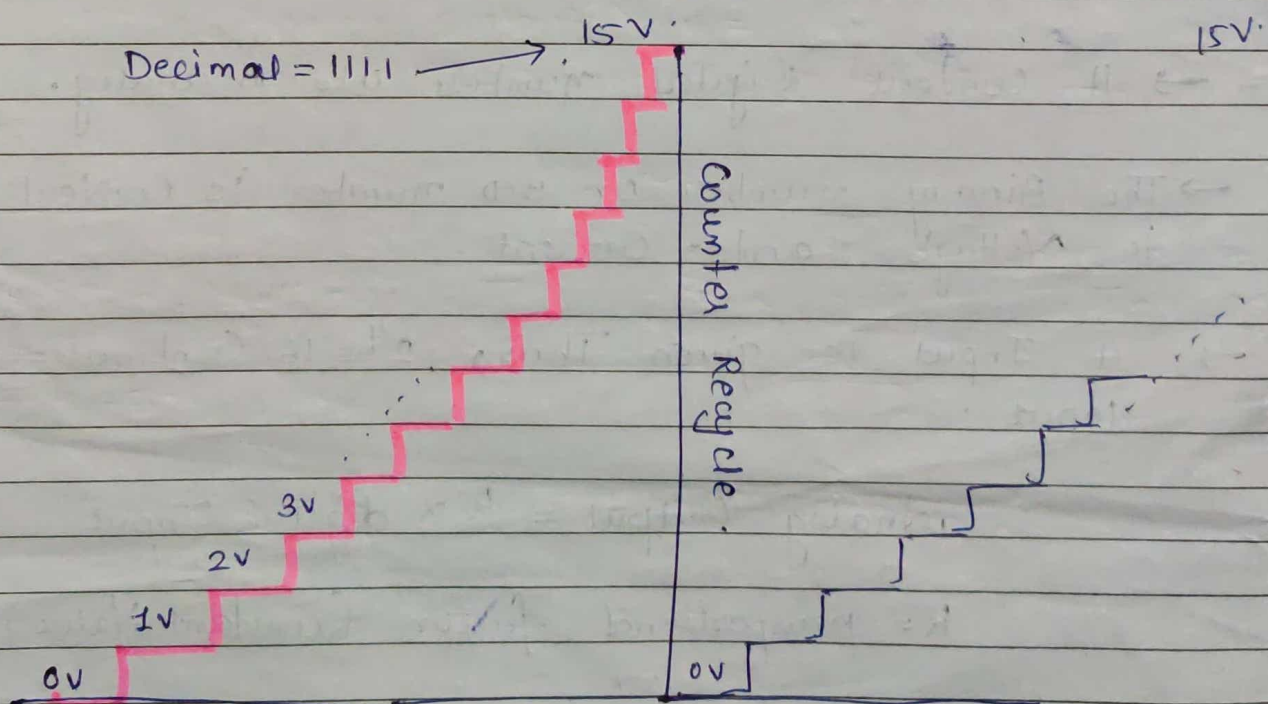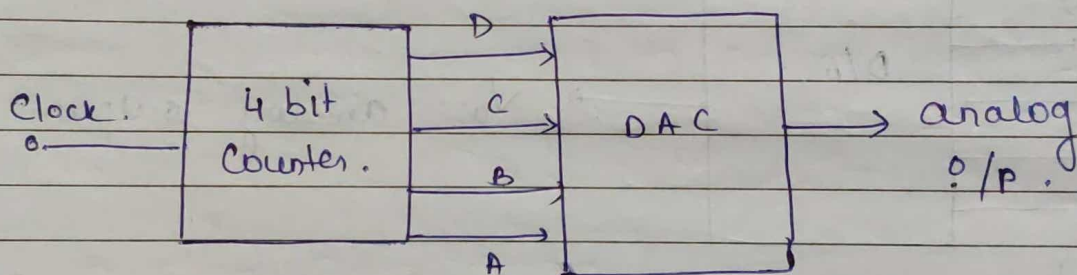

* Parameters of DAC.

1. Resolution. (step size) = .

The Smallest change that occurs in analog o/p will change digital Input.

It is Reciprocal of number of discrete steps in full-scale o/p of DAC.

$$\% \text{ Resolution} = \frac{\text{Step Size}}{\text{Full Scale}} \times 100 \%$$

$$\text{Full Scale} = \text{No. of steps} \times \text{Step Size} .$$


Step size :- difference of voltage betⁿ two values.

② Accuracy :- Defined by full scale error & linearity error in percentage

③ Settling Time :- The Settling time shows the operating speed of DAC. The time when I/p changes and the time that o/p enters a error band for the last time.

④ Offset Voltage :- When Binary I/p = 0 then o/p of DAC = 0. But if there exists a small change in output is called offset voltage.

R-2R Ladder Type DAC.

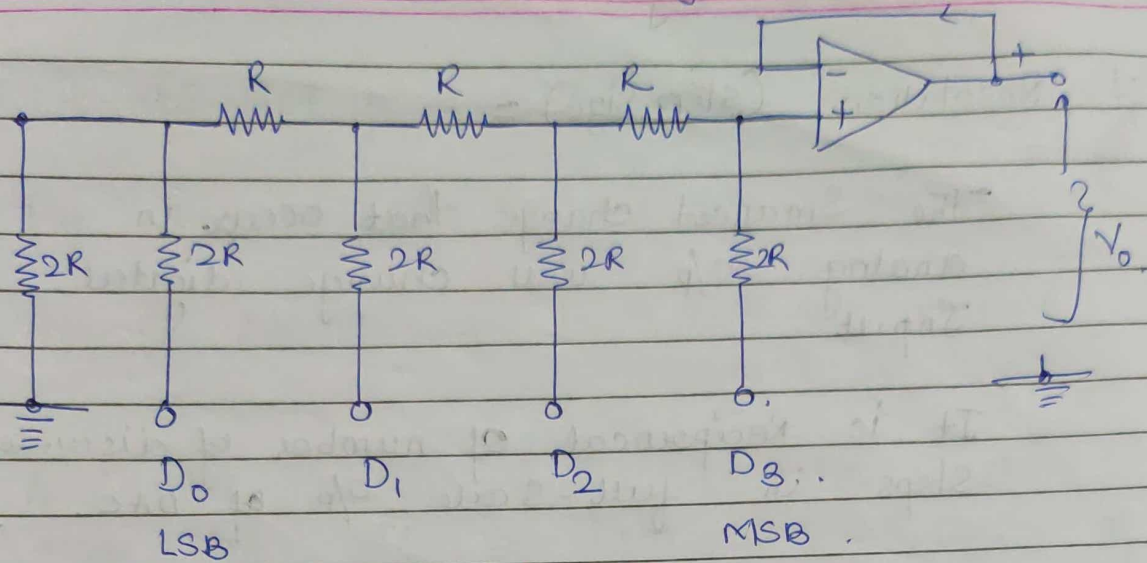

Digital I/p.

→ Most widely used.

→ Ladder NW is used i.e. Series-parallel combination of two resistor. R and $2R$.


→ Voltage follower is used to prevent loading.

→ 4 digital I/p is given through $2R$ resistor.
 $\Rightarrow D_0 \quad D_1 \quad D_2 \quad D_3$.

Eg:- when I/p = 1000 (MSB LSB).

Then Analog Output $V_{out} = ?$

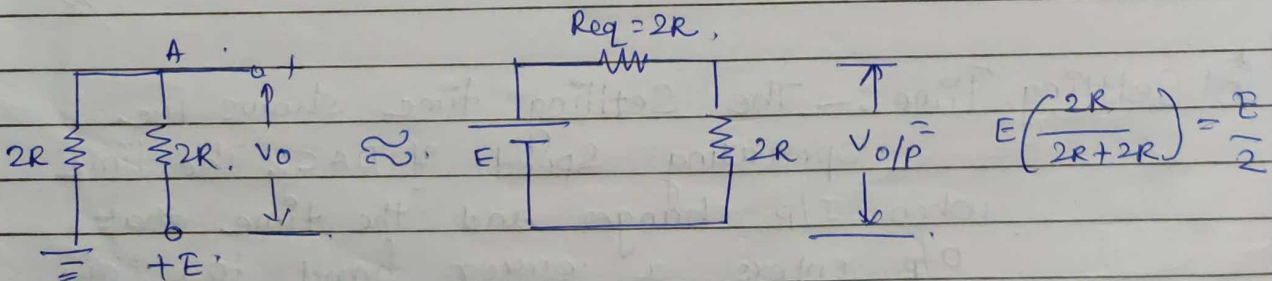$D_0 = \text{ground}, D_1 = \text{ground}, D_2 = \text{ground}, D_3 = 1$.




$$1000 = E/2 \quad ; \quad 0100 = E/4 \quad ; \quad 0010 = E/8$$

$$0001 = E/16$$

Weighted - Resistor Type DAC.

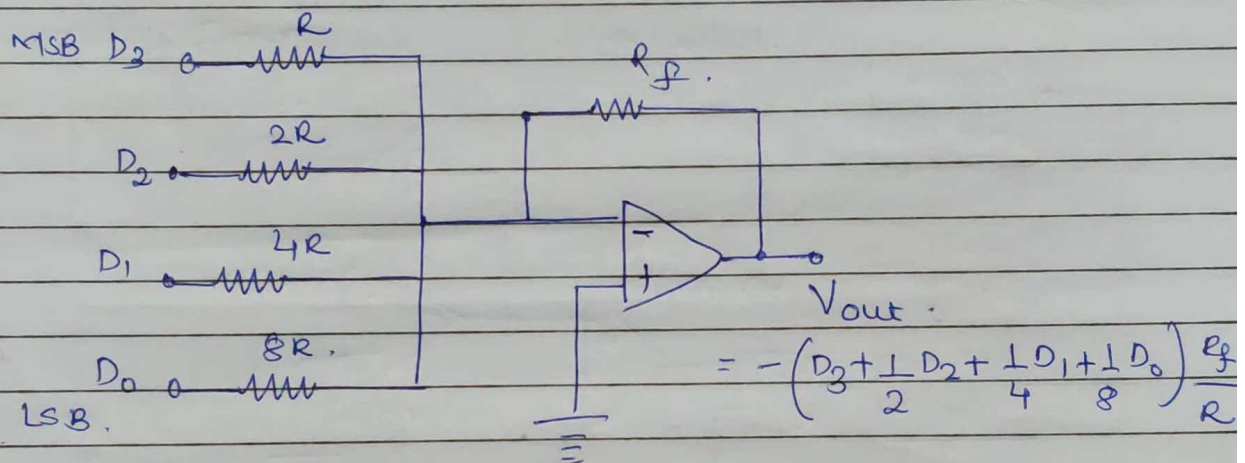- Operational amplifier is used.
- It produce weighted sum of digital input.
- Op-amp is connected as Inverting amplifier,
- Each input is amplified by Ratio of feedback Resistance divided by I/p resistance



$$D_3 = \text{amplified by } \frac{R_f}{R}$$

$$D_2 = \text{amplified by } \frac{R_f}{2R}$$

$$D_1 = \text{amplified by } \frac{R_f}{4R}$$

$$D_0 = \text{amplified by } \frac{R_f}{8R}$$

The Op-amp adds and Invert as:-

$$V_{out} = - \left[D_3 + \frac{D_2}{2} + \frac{D_1}{4} + \frac{D_0}{8} \right] \times \left[\frac{R_f}{R} \right]$$

Disadvantage :-

→ Each Resistor will be of different value for each bit position of digital input.


Analog To Digital Converter , (ADC)

Input = Analog . / output = digital .

Type of ADC

1. Dual slope
2. Successive - Approximation .
3. Specific A/D Converter .

DUAL- SLOPE A/D CONVERTER.

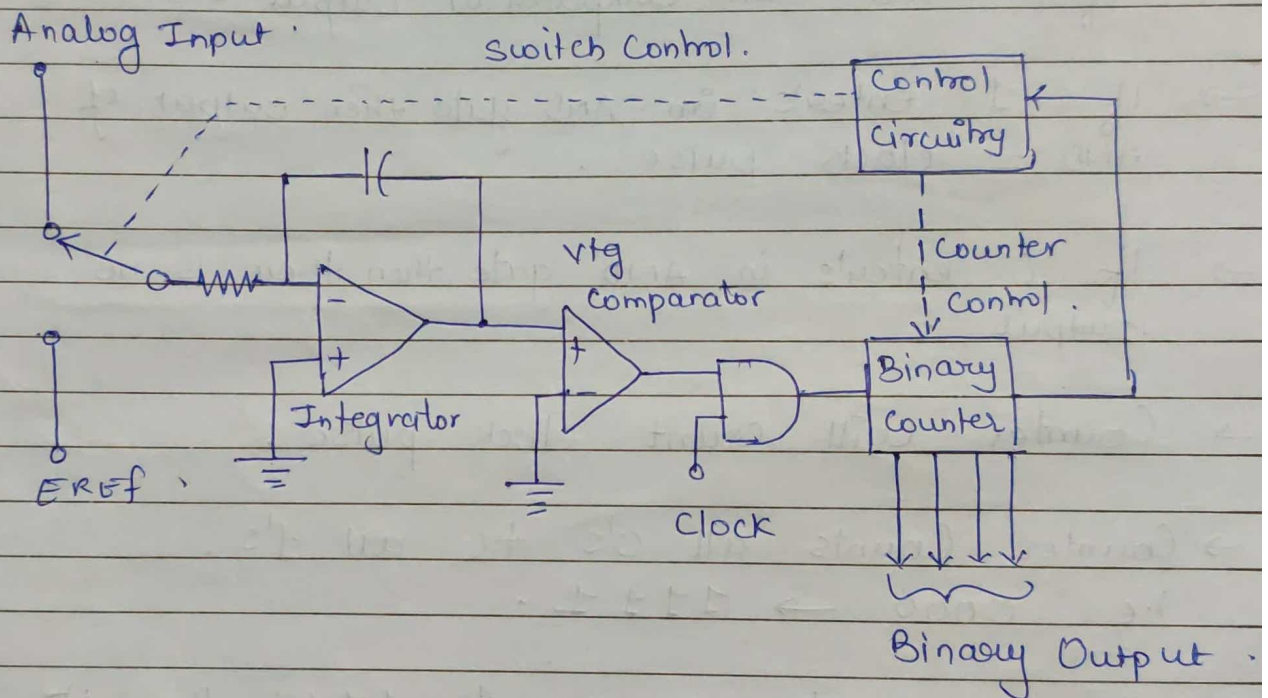

- Slowest Converter .
- Low Sensitive to Noise .
- It take large Conversion Time , It is not used in Data Acquisition application .
- It is used as Voltmeter and Multimeter .
- Input = analog .
Output = Digital .
- To Integrate Input = Operational Amplifier is used . (Integrator)
- R and C value is fixed .

- Most Accurate A/D Converter .
- Integrator Output is a ramp signal .
- V_{in} and V_{ref} polarity should be opposite with other .
 i.e If V_{in} = positive . / If V_{in} = Negative .
 then V_{ref} = Negative . / then V_{ref} = positive .

→ If $V_{in} > 0$ then Comparator output = 1 .
 If $V_{in} < 0$ then Comparator output = 0 .

→ If 1 enters in AND gate then output of AND = clock pulse .

→ If 0 enters in AND gate then there is no output .

→ Counter will count clock pulse .


→ Counter Counts all 0's to all 1's .
 i.e 0000 → 1111 .

→ Once the Counter reaches to 1111 then it restart again and the Control circuit changes the switch from V_{in} to V_{ref} .

→ Again Counter starts Counting from 0's to 1's .

Successive-Approximation ADC.

4 Bit

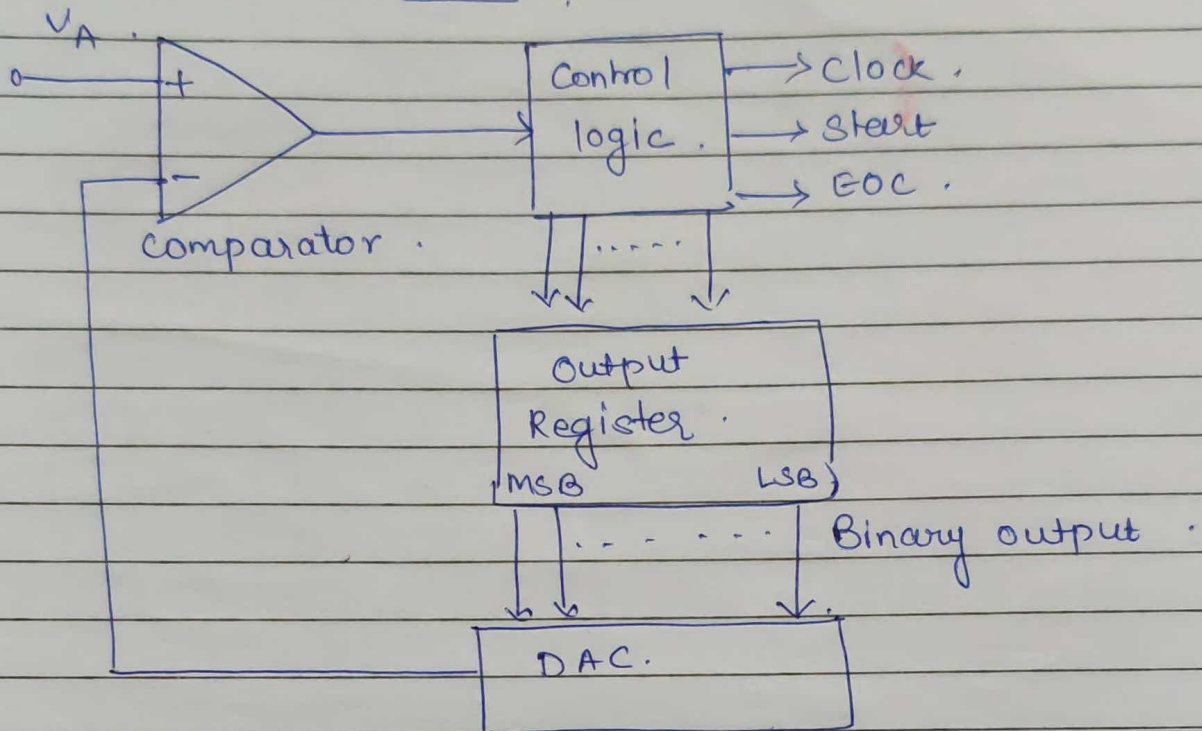

- Widely Used.
- less time to Convert the Signal from Analog to digital.
- It has fixed Conversion Time.